Exam: End_Sem_Dec-2021_CS3CO29_Digital Electronics

Digital Electronics (T)
13/30

1. Not Answered

A unit which can store a string of bits

A.	Flip flop
B.	counters
C.	Registers
D.	multiplexer

2. Correct Answer 14-Dec-2021 09:33:38 AM

The group of bits 11001 is serially shifted (right-most bit first) into a 5-bit parallel output shift register with an initial state 01110. After three clock pulses, the register contains _____

A.	1110	
B.	1	
C.	101	You Selected
D.	110	

3. Correct Answer 14-Dec-2021 09:45:22 AM

MAR stands for

A.	Main address register	
B.	Memory address register	You Selected
C.	Main accessible register	
D.	Memory accessible register	

4. Incorrect Answer 14-Dec-2021 09:31:23 AM

A _____ is a logic circuit that switches a data input toward one of the outputs depending on the selection code.

A.	Multiplexer	You Selected
B.	De-multiplexer	
C.	Encoder	
D.	Decoder	

5. Correct Answer 14-Dec-2021 09:39:19 AM

How can parallel data be taken out of a shift register simultaneously

A.	Use the Q output of the first FF	
B.	Use the Q output of the last FF	
C.	Tie all of the Q outputs together	
D.	Use the Q output of each FF	You Selected

6. Not Answered

PLD is full form of _____

A.	Programmable Large Device
B.	Programmable Long Device
C.	Programmable Logic Device
D.	Programmable Lengthy Device

7. Not Answered

Which gate is NOR/OR path?

A.	CMOS
B.	ECL
C.	TTL
D.	DTL

8. Not Answered

Which of the following numbers might represent an Octal number system?

A.	9812
B.	23A1
✓ C.	4251
D.	6318

9. Not Answered

A three input AND has fan – in as

A.	one
B.	six
✓ C.	three
D.	nine

10. Correct Answer 14-Dec-2021 09:16:42 AM

Among the following.Which ciruit's operations are more faster

✓ A.	Combinational circuits	You Selected
B.	Sequential	
C.	Latches	
D.	Flip-Flop	

11. Correct Answer 14-Dec-2021 09:28:00 AM

How many inputs will a decimal-to-BCD encoder have?

A.	4	
B.	8	
✓ C.	10	You Selected

D.	16

12. Not Answered

The reprogrammable device is

A.	ROM
B.	PAL
C.	PLA
✓ D.	PLD

13. Not Answered

Outputs of Flip-flop , are always_____

✓ A.	Complimentary
B.	same
C.	Independent of each other
D.	Same as previous Input

14. Not Answered

Which set of input is disallowed in R S Flip-flop with NAND Gates

A.	1 and 1
B.	1 and 0
✓ C.	0 and 0
D.	0 and 1

15. Not Answered

AB+A'B+BC is equal to

A.	A'B+A'C

B.	AB+A'B
✓ C.	B
D.	A'B'+A'C

16. Not Answered

What is the largest number of data inputs which a data selector with four control inputs can have?

A.	4
B.	8
✓ C.	16
D.	2

17. ✓ Correct Answer 14-Dec-2021 09:35:27 AM

Excess-3 code is _____Code.

A.	Weighted & Self complementing	
✓ B.	Un-weighted & Self complementing	✓ You Selected
C.	Weighted & not complementing	
D.	Un--weighted & not complementing	

18. ✗ Incorrect Answer 14-Dec-2021 09:18:19 AM

Number of Xor gates required for implementing Full Subtractor is_____.

✓ A.	2	
B.	3	
C.	1	✗ You Selected
D.	4	

19. Not Answered

The largest negative number in an N – bit machine is

A.	– 2(N – 1)
B.	-2N
C.	-2N-1
D.	-2N+1

20. Correct Answer 14-Dec-2021 09:38:07 AM

Radix for hexadecimal is

A.	2	
B.	8	
C.	10	
D.	16	You Selected

21. Correct Answer 14-Dec-2021 09:44:01 AM

FPGA stands for

A.	Field programmable gate array	You Selected
B.	Field process gate array	
C.	Fixed programmable gate array	
D.	Fine programmable gate array	

22. Correct Answer 14-Dec-2021 09:37:06 AM

In which of the memories, does the data disappear?

A.	SRAM

B.	DRAM	You Selected
C.	EEPROM	
D.	Flash memory	

23. Incorrect Answer 14-Dec-2021 09:29:41 AM

Transistor-Transistor Logic (TTL) based digital circuits built from

A.	BJT	You Selected
B.	FET	
C.	Diodes	
D.	BJT & Resistors	

24. Correct Answer 14-Dec-2021 09:32:53 AM

Multiplexer perform which operation?

A.	AND-OR	You Selected
B.	OR-OR	
C.	AND-AND	
D.	OR-AND	

25. Correct Answer 14-Dec-2021 09:15:47 AM

The output is false only if all the inputs are true, which gate is this ?

A.	NOR	
B.	NAND	You Selected
C.	EXOR	
D.	EXNOR	

26. Incorrect Answer 14-Dec-2021 09:32:00 AM

In the CMOS logic to implement a NAND gate the transistors must be connected in

A.	Series	
B.	Parallel	You Selected
C.	Either Series or Parallel	
D.	None of them	

27. Not Answered

How many bits are required for representation of (245)10 in binary and BCD respectively

A.	12 and12
B.	8 and 12
C.	8 and 8
D.	16 and 12

28. Correct Answer 14-Dec-2021 09:42:25 AM

The initial values in all the cells of an EPROM is _____

A.	zero	
B.	1	You Selected
C.	both 0 and 1	
D.	altenate 0 and 1	

29. Not Answered

The ECL logic family is _____than the TTL family but consumes ____energy

A.	Faster & more
B.	Slower & more
C.	Faster & less
D.	Slower & more

30. Correct Answer 14-Dec-2021 09:24:30 AM

In the TTL we use

A.	Multi emitter transistor	You Selected
B.	Multicollector Transistor	
C.	Multibase transistor	
D.	Single emitter Transistor	